


Knowledge Organiser: Electricity Y6



New Learning:


Revision of Year 4 Electricity:

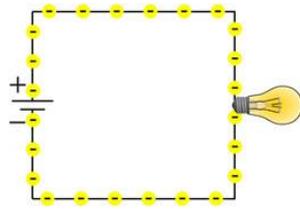- Many **common appliances** such as washing machines and televisions run on electricity.
- A **complete (closed) circuit** with a cell will allow electricity to flow around it and will switch on the bulb.




closed circuit

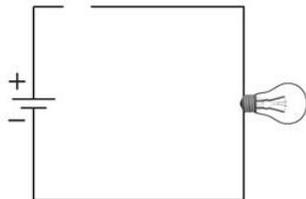- An **incomplete (open) circuit** with a cell will not allow electricity to flow and will not switch on the bulb.




- A circuit must contain a **cell** or **battery** and be closed for the components to be switched on.
- A **switch** will open or close the circuit.
- **Conductors** such as metals and graphite (pencil "lead") allow electricity to flow through them.
- **Insulators** such as wood and plastic do not allow electricity to flow through them.
- **Electricity can be dangerous** - never touch a plug or switch with wet hands. Do not go near power lines.

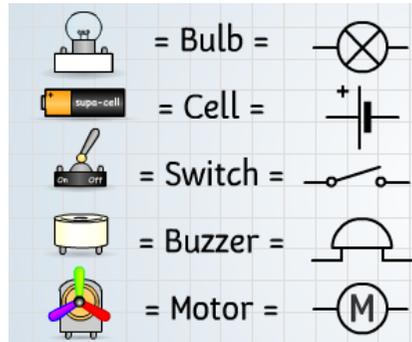- **Components** in a circuit can be represented with symbols



- Components such as a motor or buzzer are **transducers** because they change electrical energy into kinetic (movement) energy or sound energy.
- A **circuit diagram** shows all the components in a circuit and how they are connected.
- By looking at a circuit diagram we can tell whether a circuit is closed or open.
- In a **series circuit**, adding more components means the voltage is shared between them - bulbs will be dimmer and buzzers will be quieter.

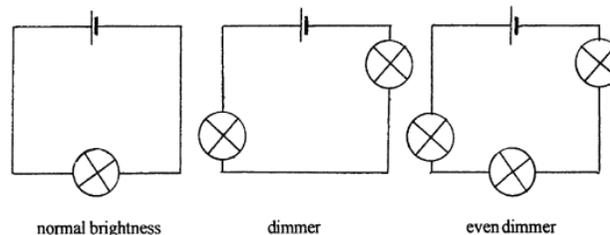

- Using a **cell with a higher voltage** will cause lamps to be brighter or buzzers to be louder.
- Using **more cells** in a series circuit will cause lamps to be brighter or buzzers to be louder.

Key Vocabulary


battery	a collection of cells. People often say 'battery' when they should say 'cell'.
cell	A device which converts chemical energy into electrical energy.
circuit	A complete route which an electric current can flow around.
component	A device in an electric circuit, such as a battery, switch or lamp.
conductor	A material that conducts electrical current because the electrons are able to move
electric current	The flow of electricity around a circuit
electrons	Negatively charged particles
insulator	A material that does not conduct electricity because the electrons are not free to move
parallel circuit	When components in a circuit have separate connections to the cell and the current (flow of electricity) is split up. Each component receives the same voltage.
resistance	The opposition in an electrical component to the movement of electrical charge through it.
series circuit	A circuit where one component follows directly from another, e.g. three bulbs in a row with no junctions are said to be connected in series. The same current flows through all components and the voltage is shared between the components.
transducer	Any device, such as a buzzer or electric motor, that converts one form of energy into another
voltage	The voltage of an electrical current is its force measured in volts.

Knowledge Organiser: Electricity Y6




Revision of Year 4 Electricity:

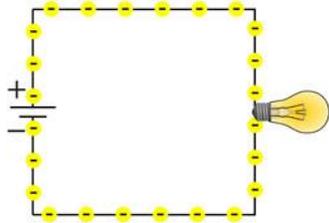- Many such as washing machines and televisions run on electricity.
- A with a cell will allow electricity to flow around it and will switch on the bulb.



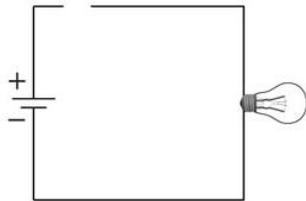
- An with a cell will not allow electricity to flow and will not switch on the bulb.




- A circuit must contain a and be closed for the components to be switched on.
- A will open or close the circuit.
- such as metals and graphite (pencil "lead") allow electricity to flow through them.
- such as wood and plastic do not allow electricity to flow through them.
- **Electricity can be dangerous** - never touch a plug or switch with wet hands. Do not go near power lines.

New Learning:

- in a circuit can be represented with

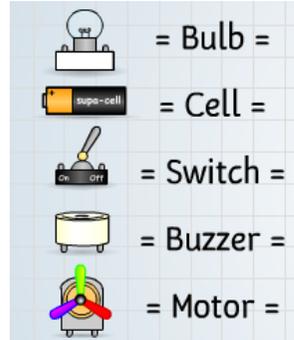

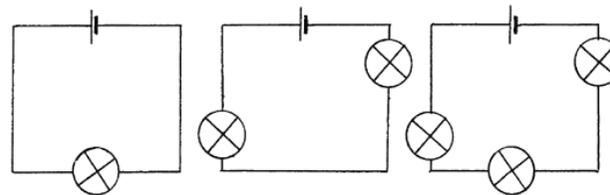- Components such as a motor or buzzer are because they change electrical energy into kinetic (movement) energy or sound energy.
- A shows all the components in a circuit and how they are connected.
- By looking at a circuit diagram we can tell whether a circuit is
- In a **series circuit**, components means the voltage is shared between them - bulbs will be dimmer and buzzers will be quieter.



- Using a **cell with a** **voltage** will cause lamps to be brighter or buzzers to be louder.
- Using **cells** in a series circuit will cause lamps to be brighter or buzzers to be louder.

Key Vocabulary

	a collection of cells. People often say 'battery' when they should say 'cell'.
	A device which converts chemical energy into electrical energy.
	A complete route which an electric current can flow around.
	A device in an electric circuit, such as a battery, switch or lamp.
	A material that conducts electrical current because the electrons are able to move
	The flow of electricity around a circuit
	Negatively charged particles
	A material that does not conduct electricity because the electrons are not free to move
	When components in a circuit have separate connections to the cell and the current (flow of electricity) is split up. Each component receives the same voltage.
	The opposition in an electrical component to the movement of electrical charge through it.
	A circuit where one component follows directly from another, e.g. three bulbs in a row with no junctions are said to be connected in series. The same current flows through all components and the voltage is shared between the components.
	Any device, such as a buzzer or electric motor, that converts one form of energy into another
	The voltage of an electrical current is its force measured in volts.